




# **COMPUTER ORGANIZATION**

## **MODULE-I (RTL, BOOTH MULTIPLIER & GRO)**

# Register, Bus and Memory Transfer
 
## Register Transfer Language:


- ✓ The operations executed on data stored in registers are called microoperations.
- ✓ The symbolic notation used to describe the microoperation transfers among registers is called **Register transfer language**.
- ✓ The term Register transfer implies the availability of hardware logic circuits to perform stated microoperation.
- ✓ Computer registers are designated by capital letters to denote the function of register.




(a) Register *R*



(b) Showing individual bits

 

(c) Numbering of bits

 

(d) Divided into two parts

## Block Diagram of Register

**Register Transfer:** The information transfer from one register to another register is designated in symbolic form.

**For example:**  $R2 \leftarrow R1$  denotes a transfer of the content of register R1 into register R2.

The above Register transfer under a predetermined control condition can be represented by an if-then statement :

$\text{If } (P=1) \text{ Then } R2 \leftarrow R1$

where P is a control signal generated in the control section.

It can be written as  $P: R2 \leftarrow R1$

### Types of Registers:

Instruction register (IR)

Program counter (PC)


General-purpose register ( $R0 - R_{n-1}$ )

Memory address register (MAR)

Memory data register (MDR)
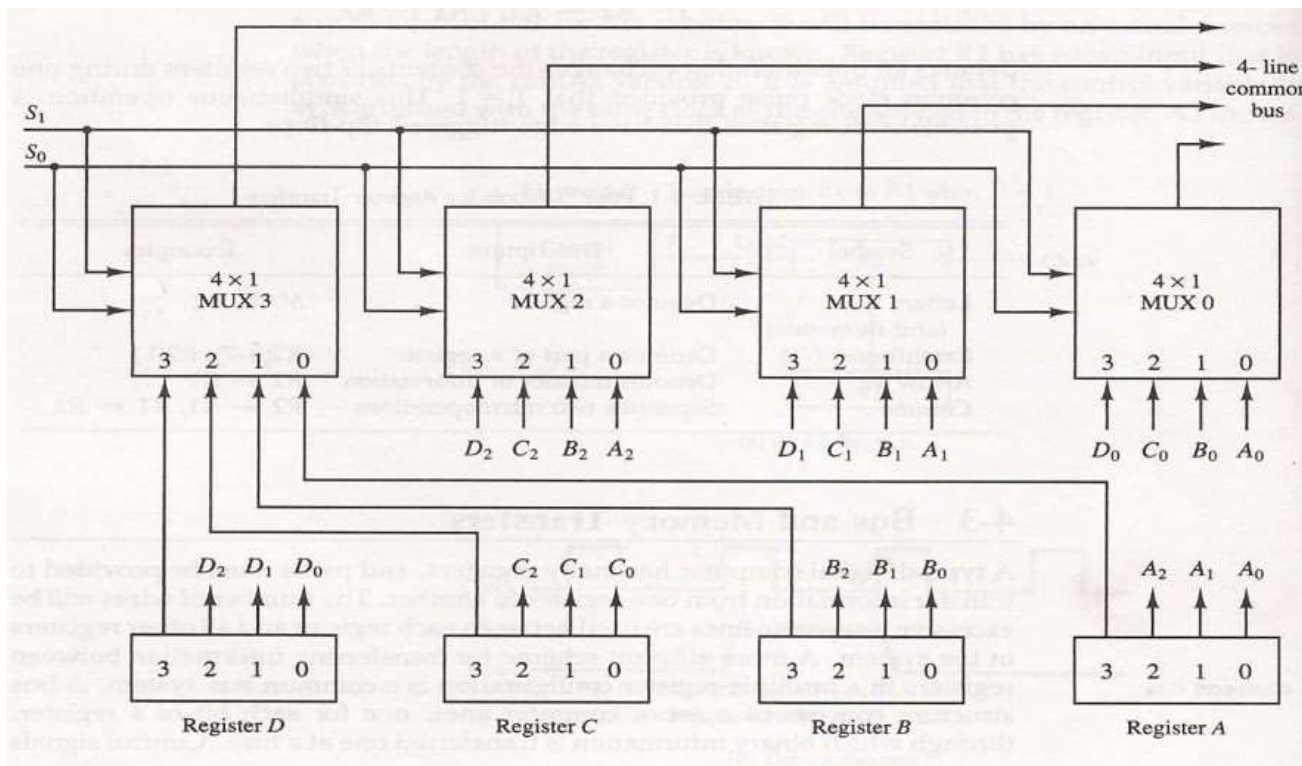
## Bus Transfer:

- ❖ A group of lines that serves as a connecting path for several devices is called a bus.
- ❖ The efficient way for transferring information between registers in a multiple-register configuration is a common system bus.
- ❖ One way of constructing a common bus system is with multiplexers which is shown in fig.



Function Table for Bus

$S_1$	$S_0$	Register selected
0	0	A
0	1	B
1	0	C
1	1	D

## Bus Transfer:

- ❖ The symbolic statement for a bus transfer may mention the bus or its presence may be implied in the statement.
- ❖ When the bus is included in the statement, the register transfer is symbolized as follows:

$$\text{BUS} \leftarrow C, \quad R1 \leftarrow \text{BUS}$$

- ❖ The content of register C is placed on the bus and the content of the bus is loaded into register R1 by activating its load control input.
- ❖ If the bus is known to exist in the system, it may be convenient just to show the direct transfer.

$$R1 \leftarrow C$$

## Three-state Bus Buffers:


- ❖ Two of the states are signals equivalent to logic 1 and 0 as in a conventional gate.
- ❖ The third stage is a high-impedance state which behaves like an open circuit.
- ❖ The most commonly used in the design of a bus system is the buffer gate.

## Problem:

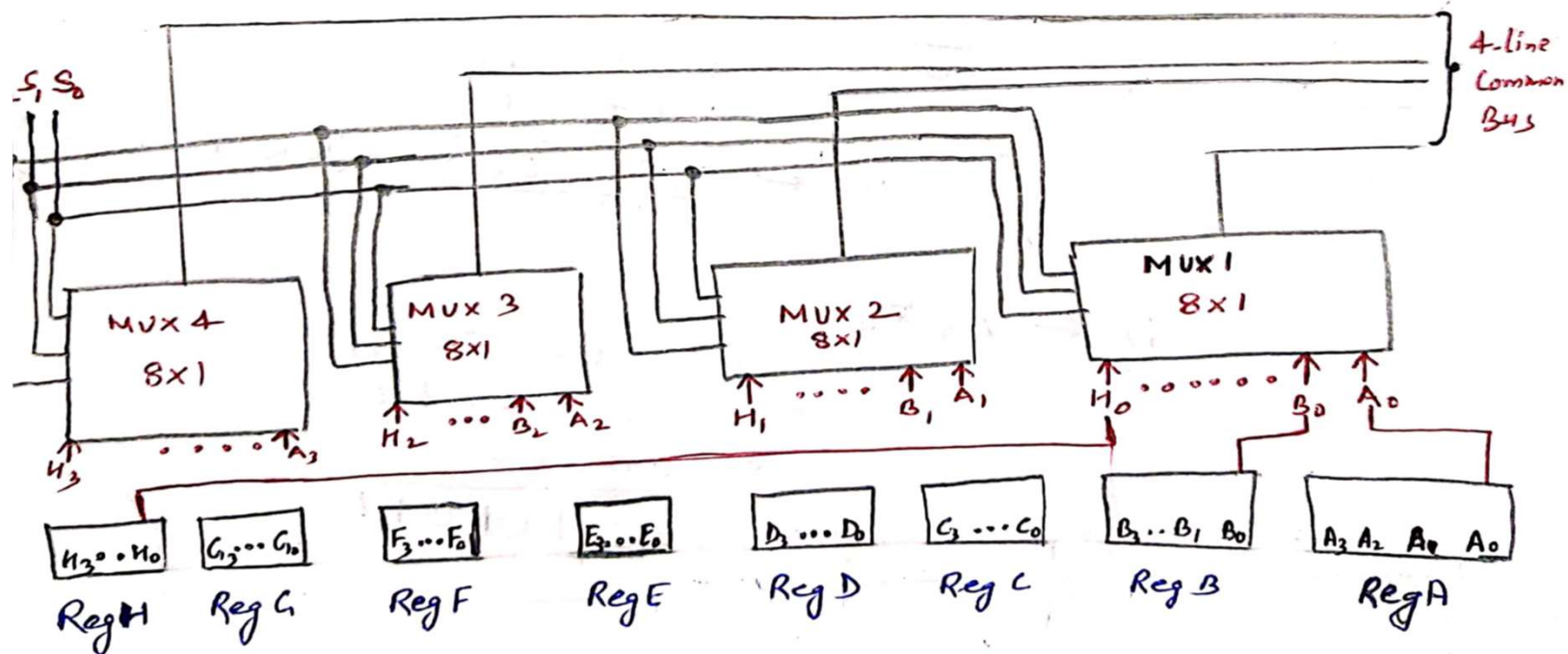1. A bus organization has eight 4-bit registers. Show, how multiplexers can be used to select registers in a common bus configuration?

Answer:

Here, No. of MUX = No. of bits in each register = 4  
Size of MUX = No. of register used  $\times 1 = 8 \times 1$   
Select lines for each MUX = 3 ( $\because 8 = 2^3$ )



## Memory Transfer:

- The transfer of information from a memory word to the outside environment is called a **read** operation.
- The transfer of new information to be stored into the memory is called a write operation.
- A memory word will be symbolized by the letter M.
- Consider a memory unit that receives the address from a register called address register (AR) and data transferred to another register called data register (DR).
- The read operation can be symbolized by:

**Read :  $DR \leftarrow M[AR]$**

- This causes a transfer of information into DR from the memory word M selected by the address in AR.
- The write operation transfers the content of a data register like R1 to memory word M selected by address.


**Write:  $M[AR] \leftarrow R1$**

- This causes a transfer of information from R1 into the memory word M selected by the address in AR.
 
## Binary (Array) Multiplier:

- Multiplication of binary numbers is performed in the same way as multiplication of decimal numbers.
- The multiplicand is multiplied by each bit of the multiplier, starting from the least significant bit.

$$\begin{array}{r} \begin{array}{cc} B_1 & B_0 \\ \hline A_1 & A_0 \\ \hline A_0B_1 & A_0B_0 \end{array} \\ \begin{array}{cc} A_1B_1 & A_1B_0 \\ \hline C_3 & C_2 & C_1 & C_0 \end{array} \end{array}$$



Two-bit by two-bit binary multiplier




# Booth's Algorithm


- ✓ Booth algorithm gives a procedure for multiplying binary integers in signed-2's complement representation.
- ✓ As in all multiplication schemes, Booth algorithm requires examination of the multiplier bits and shifting of the partial product.
- ✓ Prior to the shifting, the multiplicand may be added to the partial product, subtracted from the partial product, or left unchanged according to the following rules:
  1. The multiplicand is subtracted from the partial product upon encountering the first least significant 1 in a string of 1's in the multiplier.
  2. The multiplicand is added to the partial product upon encountering the first 0 (provided that there was a previous 1) in a string of 0's in the multiplier.
  3. The partial product does not change when the multiplier bit is identical to the previous multiplier bit.
- ✓ The algorithm works for positive or negative multipliers in 2's complement representation. This is because a negative multiplier ends with a string of 1's and the last operation will be a subtraction of the appropriate weight.
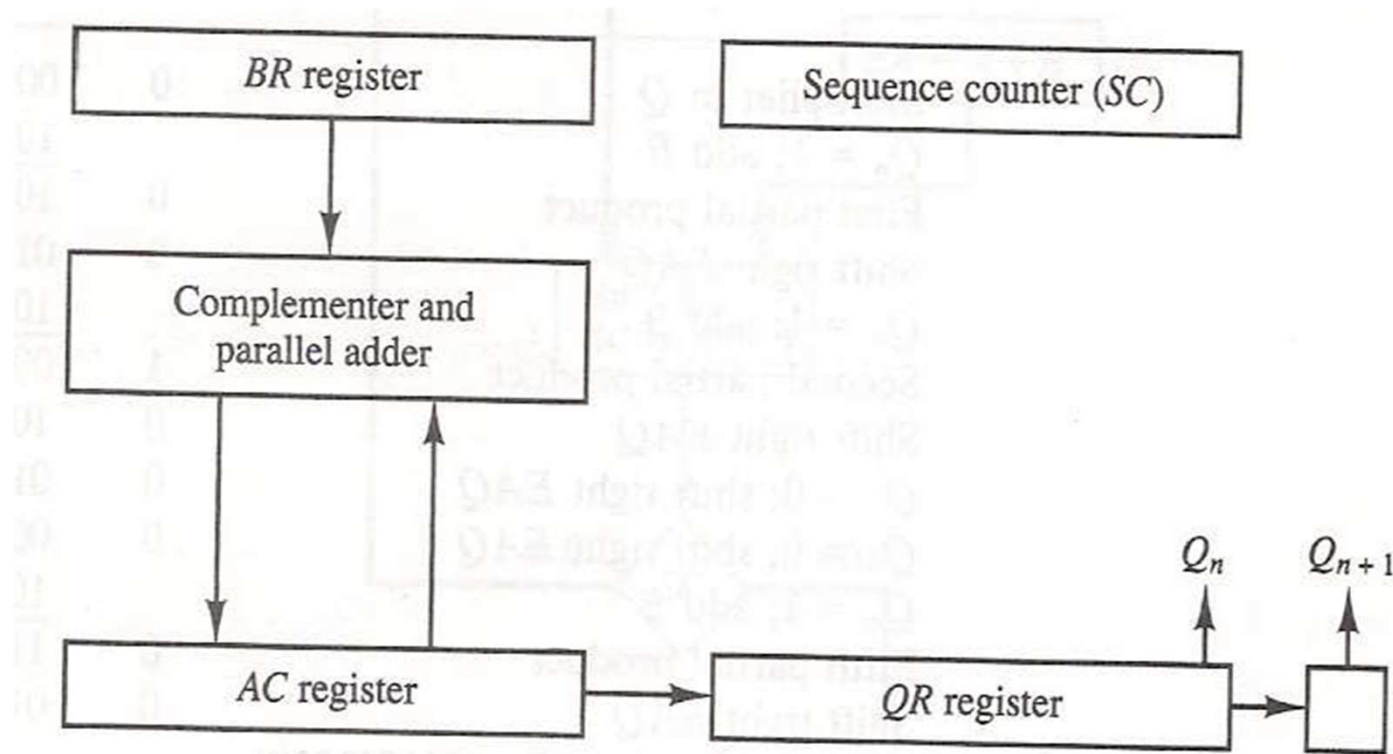
# Hardware Implementation of Booth's Algorithm:

- The sequence counter SC is initially set to a number equal to the number of bits in the multiplier. The counter is decremented by 1 after forming each partial product. When the content of the counter reaches zero, the product is formed and the process stops.
- The multiplier and multiplicand are stored in the QR and BR registers respectively.  $Q_n$  designates the least significant bit of the multiplier in register QR. An extra flip-flop  $Q_{n+1}$  is appended to QR to facilitate a double bit inspection of the multiplier.



# Flowchart of Booth's Algorithm:

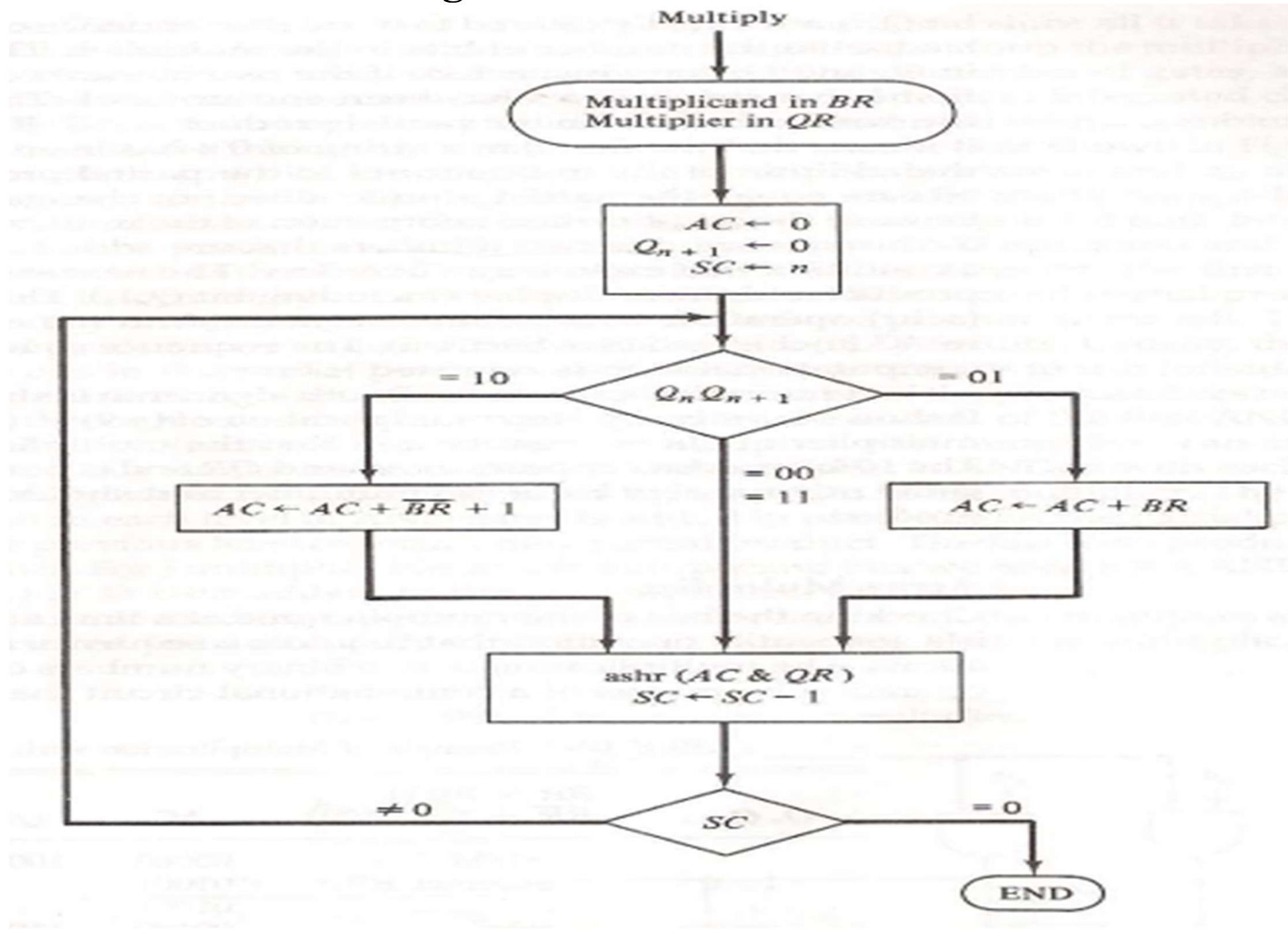

# Flowchart of Booth's Algorithm:

- ❖ AC and the appended bit  $Q_{n+1}$  are initially cleared to 0 and the sequence counter SC is set to a number  $n$  equal to the number of bits in the multiplier.
- ❖ The two bits of the multiplier in  $Q_n$  and  $Q_{n+1}$  are inspected.
- ❖ If the two bits are equal to 10, it means that the first 1 in a string of 1's has been encountered. This requires a subtraction of the multiplicand from the partial product in AC.
- ❖ If the two bits are equal to 01, it means that the first 0 in a string of 0's has been encountered. This requires the addition of the multiplicand to the partial product in AC.
- ❖ When the two bits are equal, the partial product does not change. An overflow cannot occur because the addition and subtraction of the multiplicand follow each other. As a consequence, the two numbers that are added always have opposite signs, a condition that excludes an overflow.
- ❖ The next step is to shift right the partial product and the multiplier (including bit  $Q_{n+1}$ ). This is an arithmetic shift right (ashr) operation which shifts AC and QR to the right and leaves the sign bit in AC unchanged. The sequence counter is decremented and the computational loop is repeated  $n$  times.

# Example of Booth's Algorithm:


- ❖ Example below shows the multiplication of **-9** and **-13** by Booth's Algorithm.  
 ( **-9**) x ( **-13**) = **+117** (**-9** = **Multiplicand BR**, **-13** = **Multiplier QR**, **Q<sub>n</sub>**= **LSB of QR**)  
 (-9 2's complement = 10111, -13 2's complement = 10011) (SC = n = 5 = 101)
- ❖ The multiplier in QR is negative and that the multiplicand in BR is also negative. The 10-bit product appears in AC and QR and is positive. The final value of Q<sub>n+1</sub> is the original sign bit of the multiplier and should not be taken as part of the product.

$Q_n Q_{n+1}$		$BR = 10111$ $\overline{BR} + 1 = 01001$	AC	QR	$Q_{n+1}$	SC
		Initial	00000	10011	0	101
1	0	Subtract $BR$	01001			
			<u>01001</u>			
		ashr	00100	11001	1	100
1	1	ashr	00010	01100	1	011
0	1	Add $BR$	10111			
			<u>11001</u>			
		ashr	11100	10110	0	010
0	0	ashr	11110	01011	0	001
1	0	Subtract $BR$	01001			
			<u>00111</u>			
		ashr	00011	10101	1	000

❖ Final value = 00011 10101 = 1110101 = (117)<sub>10</sub>
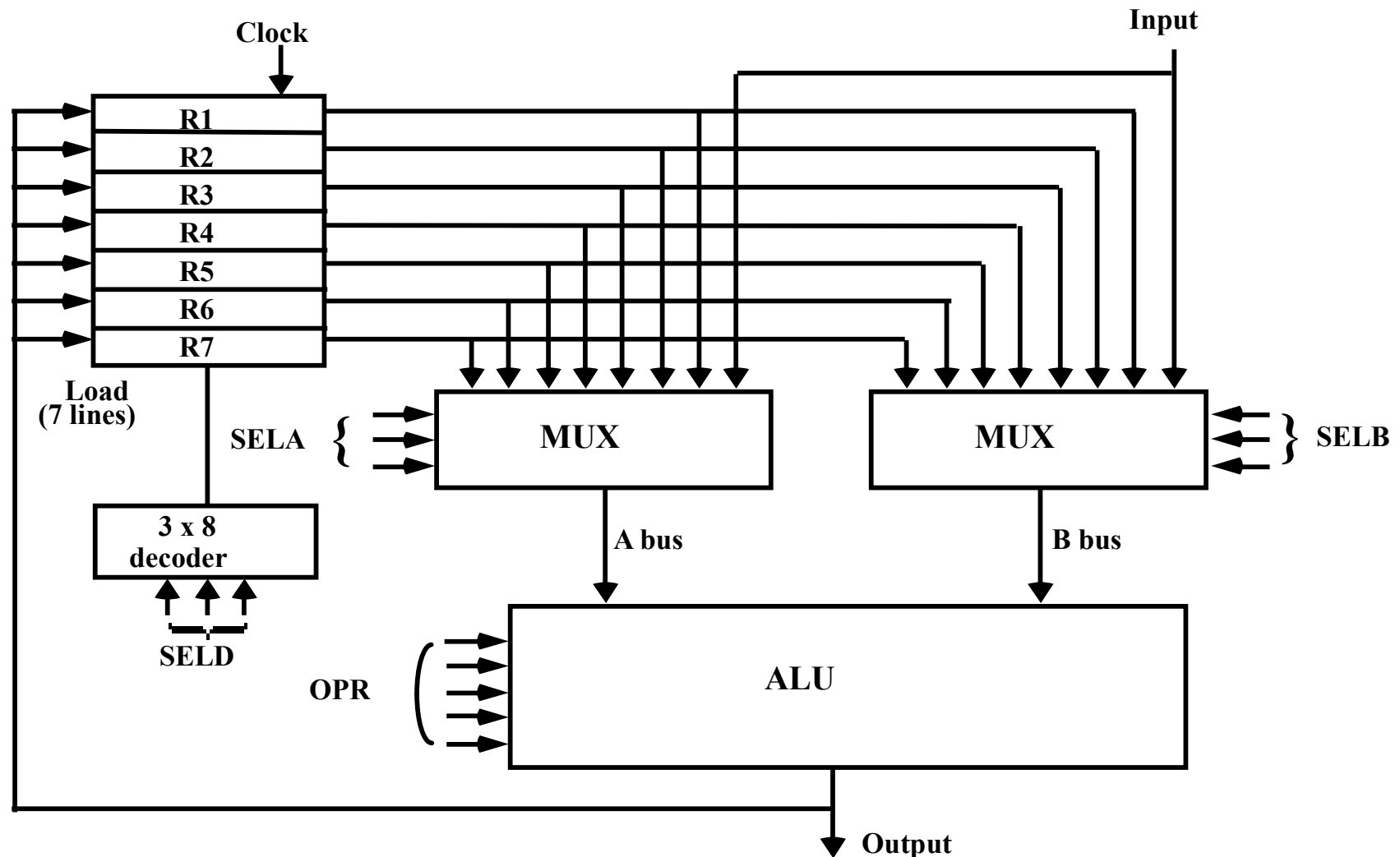
# General Register Organization

- ❖ When a large number of registers are included in the CPU, it is most efficient to connect them through a common bus system. SELA, SELB, SELD OPR are control word.



## Operation of Control Unit:

- ✓ The control unit directs the information flow through the registers and ALU by selecting various components in the system

**Example:**  $R1 \leftarrow R2 + R3$

The control must provide binary selection variables to the following selector inputs:

- [1] MUX A selector (SELA):  $BUS\ A \leftarrow R2$
- [2] MUX B selector (SELB):  $BUS\ B \leftarrow R3$
- [3] ALU operation selector (OPR): ALU to ADD
- [4] Decoder destination selector (SELD):  $R1 \leftarrow Output\ Bus$

Control Word (14 bit):	3	3	3	5
	SELA	SELB	SELD	OPR

Encoding of register selection fields:

Binary Code	SELA	SELB	SELD
000	Input	Input	None
001	R1	R1	R1
010	R2	R2	R2
011	R3	R3	R3
100	R4	R4	R4
101	R5	R5	R5
110	R6	R6	R6
111	R7	R7	R7

## ALU Unit:

Encoding of ALU operations:

OPR Select	Operation	Symbol
00000	Transfer A	TSFA
00001	Increment A	INCA
00010	ADD A + B	ADD
00101	Subtract A - B	SUB
00110	Decrement A	DECA
01000	AND A and B	AND
01010	OR A and B	OR
01100	XOR A and B	XOR
01110	Complement A	COMA
10000	Shift right A	SHRA
11000	Shift left A	SHLA

Examples of ALU Microoperations:

Microoperation	Symbolic Designation				Control Word
	SELA	SELB	SELD	OPR	
$R1 \leftarrow R2 - R3$	R2	R3	R1	SUB	010 011 001 00101
$R4 \leftarrow R4 \vee R5$	R4	R5	R4	OR	100 101 100 01010
$R6 \leftarrow R6 + 1$	R6	-	R6	INCA	110 000 110 00001
$R7 \leftarrow R1$	R1	-	R7	TSFA	001 000 111 00000
$\text{Output} \leftarrow R2$	<u>R2</u>	-	None	TSFA	010 000 000 00000
$\text{Output} \leftarrow \text{Input}$	<u>Input</u>	-	None	TSFA	000 000 000 00000
$R4 \leftarrow \text{shl } R4$	R4	-	R4	SHLA	100 000 100 11000
$R5 \leftarrow 0$	R5	R5	R5	XOR	101 101 101 01100




## Problem:

1. Considering the GRO configuration, write the RTL statement of the micro-operation which will be executed upon the control unit's generation of the control word 01101000100101.
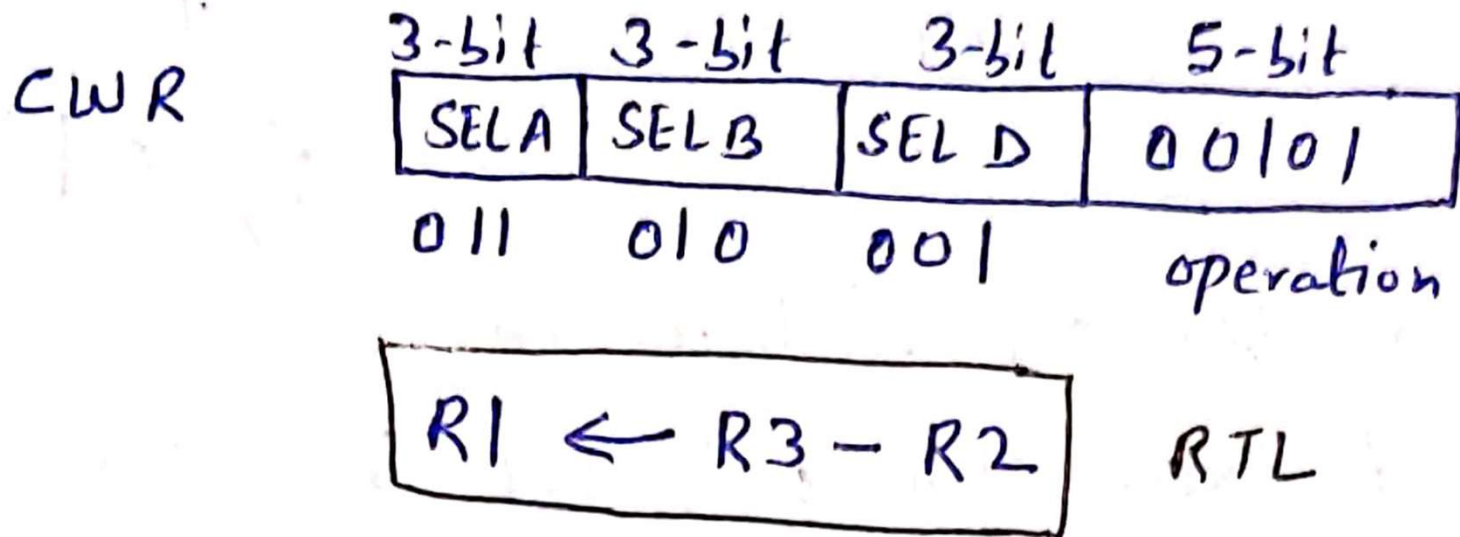
## Answer:

Control word is given 01101000100101

RTL: SUB R1, R3, R2 ( $R1 \leftarrow R3 - R2$ )



# Stack Organization:

Stack:

- Efficient for arithmetic expression evaluation
- Storage which can be accessed in LIFO
- Pointer: SP (which holds the address for the stack is called stack pointer)
- Only PUSH (Insertion) and POP (Deletion) operations are applicable

Ex: 64-word stack, the SP contains 6 bits.

Register Stack

Push, Pop operations

**/\* Initially, SP = 0, EMPTY = 1, FULL = 0 \*/**

## PUSH

**$SP \leftarrow SP + 1$**

**$M[SP] \leftarrow DR$**

**If (SP = 0) then (FULL  $\leftarrow$  1)**

**EMPTY  $\leftarrow$  0**


## POP

**$DR \leftarrow M[SP]$**

**$SP \leftarrow SP - 1$**

**If (SP = 0) then (EMPTY  $\leftarrow$  1)**

**FULL  $\leftarrow$  0**

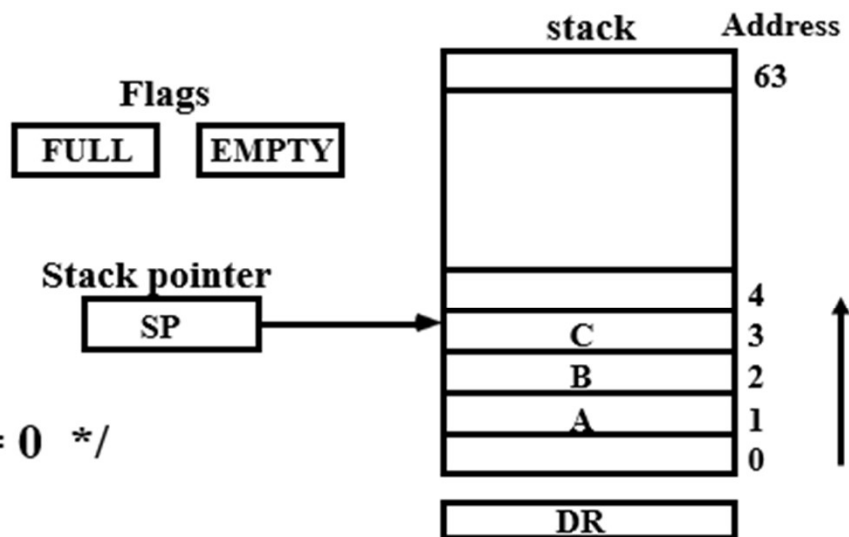

## Memory Stack:

- ✓ The implementation of a stack in the CPU is done by assigning a portion of memory to a stack operation and using a processor register as a stack pointer.
- ✓ Push operation:

$$\begin{aligned} SP &\leftarrow SP - 1 \\ M[SP] &\leftarrow DR \end{aligned}$$

- ✓ POP operation:

$$\begin{aligned} DR &\leftarrow M[SP] \\ SP &\leftarrow SP + 1 \end{aligned}$$

# ***THANK YOU***

